



# ASVAB-SECTION-5<sup>Q&As</sup>

ASVAB Section Five : Electronic Information

**Pass ASVAB ASVAB-SECTION-5 Exam with 100% Guarantee**

Free Download Real Questions & Answers **PDF** and **VCE** file from:

<https://www.passapply.com/asvab-section-5.html>

100% Passing Guarantee  
100% Money Back Assurance


Following Questions and Answers are all new published by ASVAB  
Official Exam Center

- ⚙ **Instant Download** After Purchase
- ⚙ **100% Money Back** Guarantee
- ⚙ **365 Days** Free Update
- ⚙ **800,000+** Satisfied Customers





QUESTION 1

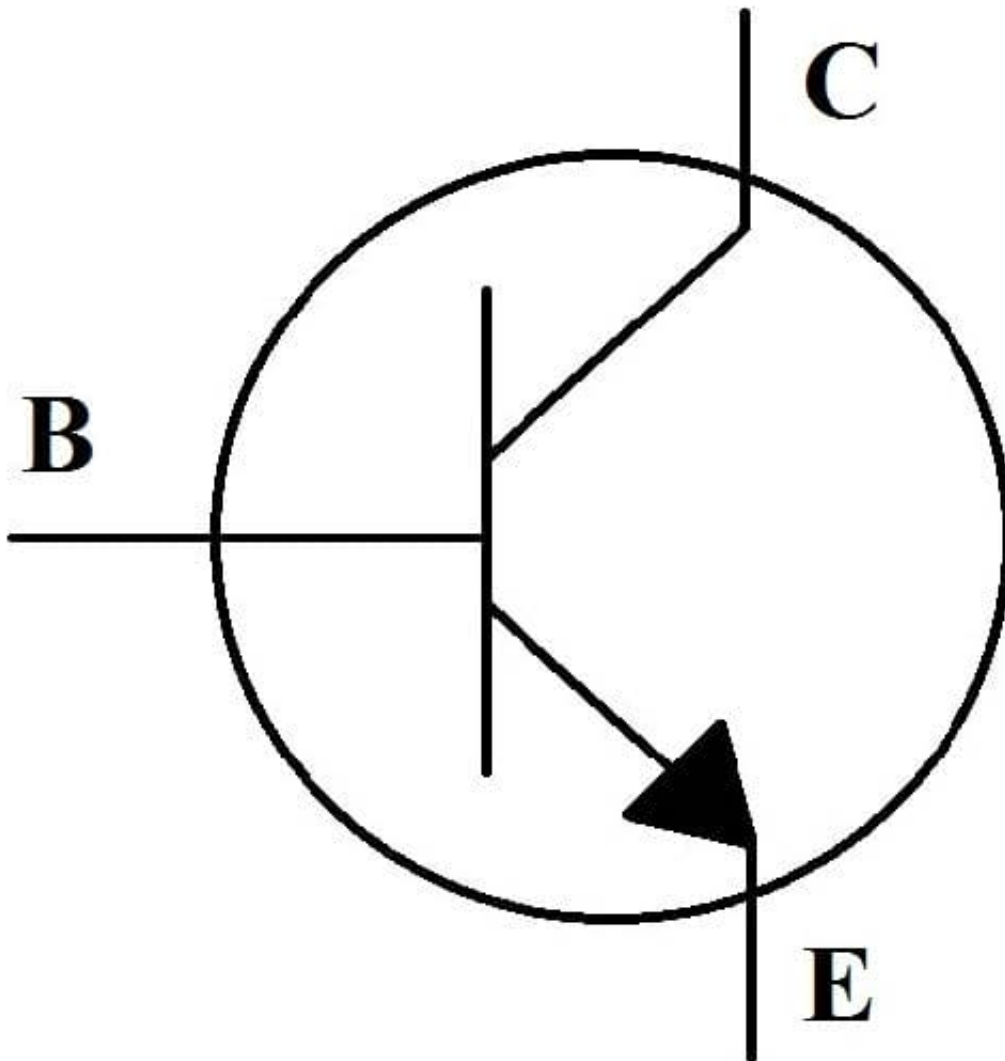

This symbol represents what electronic circuit component?

- A. power source
- B. load
- C. transistor
- D. conductor

Correct Answer: C

QUESTION 2

The rate of electrons through a conductor is measured in units of \_\_\_\_\_.



- A. current
- B. electricity
- C. volts
- D. amperes

Correct Answer: D

---

### QUESTION 3

How much power is being carried in a 220-volt circuit when the current is 10 amps?

- A. 22 watts
- B. 220 watts
- C. 2,200 watts
- D. 4,400 watts

Correct Answer: C

How much power is being carried in a 220-volt circuit when the current is 10 amps? 2,200 watts (220 volts multiplied by 10 amps = 2,200 watts).

---

### QUESTION 4

How many volts does it take to send 99 amps of current through 99,000 ohms of resistance?

- A. 0.009801 volts
- B. 980.1 megavolts
- C. 9.801 megavolts
- D. 98.01 volts

Correct Answer: C

---

### QUESTION 5

A resistor marked 2.5K ohms has the value of \_\_\_\_\_.

- A. 2.5 ohms
- B. 250 watts
- C. 2,500 ohms



D. 25,000 ohms

Correct Answer: C

2.5K ohms is 2,500 ohms. K = one kilo or 1,000.

[Latest ASVAB-SECTION-5  
Dumps](#)

[ASVAB-SECTION-5 PDF  
Dumps](#)

[ASVAB-SECTION-5  
Practice Test](#)